



Principle document of A simple low power

DC-DC boost converter

Very often a low power boost converter used to convert some low voltage to a higher voltage is required in a system. This build exercise is to learn to build one such simple converter, using an open loop. Open loop implies that we will not use output voltage as feedback, as it gives fixed voltage.

Let us take a 5V DC input and lets us assume we need a 12V DC output, say up to 1Amp output current as shown in Fig1



The circuit consists of an inductor, a MOSFET (switch), a diode (D) and a capacitor(C). The MOSFET switch is turned ON and OFF at higher frequency, say at 20 KHz. Two more parameters are required to build the circuit, Let the output voltage be Vo and the output current be Io, the output will have ripples, which is Δ Vo and Δ Io respectively.





Thus, the specification of the converter is: Vs = Input supply voltage, say 5V Vo = Output voltage, say 12V Io = Output current, say 1Amp $\triangle Io = Output ripple current, say 10% of Io$ $\triangle Vo = Output ripple voltage, say 10% of Vo$ $V_L = Inductor voltage$ $I_L = Inductor current$ $\triangle I_L = 10\%$ of Inductor current $F_m = Frequency$ T = Total period Po = output powerPin = input power

A circuit to build a converter is shown in fig. 2. As mentioned, MOSFET will be switched ON and OFF at frequency F_m , with on time Ton and off time Toff.

Thus, Ton+Toff = $\frac{1}{Fm}$

And duty cycle $D = \frac{Ton}{Ton+Toff}$

One must obtain the values of D, L and C to need the desired specs.





How does a converter work?

1. <u>During MOSFET ON period</u>, the circuit required is in Fig2. The diode represents two circuits, with Vs discharging through inductor and MOSFET as one and the capacitor discharging through load as another.





We get,

 $V_L = V_S$, and $L\frac{di_1}{dt} = V_S$ or $di_1 = \frac{V_S}{L} dt$ Integrating both side

$$\Delta I_L = \frac{V_s}{L} \int_0^{Ton} dt$$

Principle document





$$\Delta I_L = \frac{V_s}{L} \text{Ton} \dots \text{eqn} (1)$$
As Ton = DT, and T= $\frac{1}{F_m}$

$$\Delta I_L = \frac{V_s D}{L F_m} \dots \text{eqn} (2)$$
As, Po = Pin

power supplied by the source must be the same as the power absorbed by the load. Hence

Vo Io = Vs
$$I_L$$

 $I_L = \frac{Vo Io}{Vs}$

Assume that it is not desirable to have ΔI_L higher than ΔI_o , which is 10% of Io. With that assumption, we are taking ΔI_L is 10% of I_L . Now using eqn(2) we can compute L

$$L = \frac{DV_S}{F_m \Delta I_L}$$

Let us now look at capacitor discharged through load, R

The discharge is $Q = Io \times Ton = \frac{Vo \times Ton}{R}$

Where R is load resistance. Thus, the voltage Vo will drop

$$\Delta Vo = \frac{Q}{C} \text{ or } \frac{\text{Vo} \times \text{Ton}}{\text{RC}} \text{ or } \frac{\text{Vo} \times \text{DT}}{\text{RC}} \text{ , or}$$
$$\Delta Vo = \frac{\text{Vo} \times \text{D}}{\text{RCF}_{\text{m}}} = \text{output ripple voltage}.....eqn (3)$$
In otherwards,

$$\Delta Io \times R = \frac{Io \times D}{CF_{m}}$$
 or,

Principle document





$$\Delta Io = \frac{Io \times D}{RCF_{m}} = \text{output ripple current....eqn (4)}$$

From eqn (2),

$$\frac{\Delta Vo}{Vo} = \frac{D}{RCF_{m}}$$

From maximum load, we can compute C:

$$C = \frac{Vo \times D}{\Delta VoRF_m}$$

For, higher load (lower output pulse), ripple will always be less.

2. <u>During MOSFET OFF</u>: The circuit is given by Fig.3 the current I_L now will fall as shown in Fig.4 - 4(b).



Fig.3







$$V_L = (V_o - V_S), \text{ or}$$

$$L\frac{\text{di}_L}{\text{dt}} = (Vo - Vs) \dots \text{eqn } (5),$$

$$\Delta I_L = \frac{(V_o - V_S)}{L} \int_{\text{Ton}}^{\text{Ton+Toff}} \text{dt}$$

$$\Delta I_L = \frac{(V_o - V_S) \text{Toff}}{L} \dots \text{eqn } (6),$$

During steady state, the fall ΔI_L given in eqn (6), must be same as the rise ΔI_L during ON period given in eqn (1). Thus

This can be used to compute D required to obtain the required output voltage.





Summarizing all the formulas:

$$Vo = \frac{V_{S}}{1-D}$$
$$L = \frac{DV_{S}}{F_{m}\Delta I_{L}}$$
$$C = \frac{VoD}{\Delta VoRF_{m}}$$

Calculations: According to the specs of the converter, calculating D, L and C

$$D = 1 - \frac{5}{12} = 0.58 = 58 \%$$
$$L = \frac{0.58 \times 5}{20 \text{ KHZ} \times 0.24} = 0.6 \text{mH}$$
$$C = \frac{12 \times 0.58}{12 \times 1.2 \times 20 \text{khz}} = 24.16 \mu \text{F}$$

Losses

There are four types of losses:

- a. Switching loss
- b. Conduction loss
- c. Inductor loss
- d. Diode loss





Thus, the specification for calculating losses is:

- $t_r = rise time of MOSFET, says 98ns$
- $t_f = fall time of MOSFET, says 21ns$
- R_{DS} = drain to source resistance of MOSFET, says 3.7milli ohm
- R_L = internal Inductor resistance, says 3 mH
- P_o = output power, says 12 watts

 V_f = forward voltage of diode, says 0.7V

 $P_{total \, losses} = sum of all \, losses$

Note: These parameters depend on components datasheet.

 $P_{switching loss} = \frac{V_L I_L(t_r + t_f)F_m}{6}$ $P_{conduction loss} = I_L^2 R_{DS} D$ $P_{inductor loss} = I_L^2 R_L D$ $P_{Diode loss} = V_f I_L(1 - D)$ $Efficiency = \frac{P_o}{P_o + P_{Total losses}} \times 100\%$

Steps for designing boost converter with the help of Dexter Board

- 1. Design a Boost converter circuit on zero dot board.
- 2. Drive the switching device (MOSFET) with the help of the Dexter board.
- 3. Use STM32CUBE IDE for generating PWM.
- 4. Supply voltage = 5Volt, Supply frequency = 20kHZ





Principle document

10