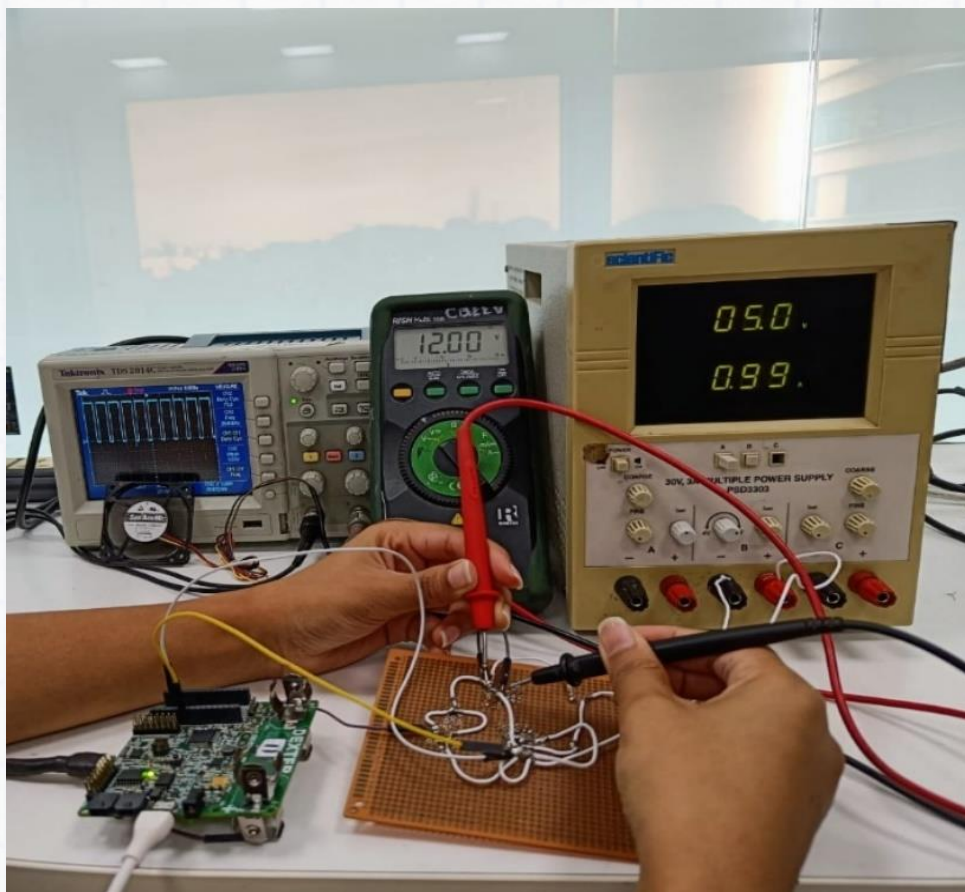


# Build a simple low power DC-DC boost converter



|                                       |   |
|---------------------------------------|---|
| Introduction to the course:           | Very often a low power boost converter is used to convert low voltage to a higher voltage is required in a system. This build exercise is to learn to build one such simple converter, using an open loop.        |
| What does this course aim to achieve? | <ul style="list-style-type: none"> <li>• To drive an LED</li> <li>• To drive a single lithium-ion cell from low volt to high volt.</li> <li>• To drive automotive device such as a fan from 5V to 12 V</li> </ul> |
| What is being built in this course:   | Boost converter (5V DC input to 12V DC output).   |
| How is it being tested:               | Based on the design requirements, the components are mounted on dot board. With the required input supply, the output results are monitored using multimeter.   |
| Course Prerequisites                  | <ul style="list-style-type: none"> <li>• Principle of boost converter</li> <li>• Basics of RLC circuits</li> <li>• Soldering techniques</li> </ul>  |



## Contents

Prerequisites

Aim

Components

Connections - Circuit Diagram - Detailed Steps

Software - Launching the IDE for our project - Code

Task - Exercise

## Prerequisites

| Topic   | Resources   |
|---|---|
| Soldering technique                             | <a href="https://youtu.be/oqV2xU1fee8">https://youtu.be/oqV2xU1fee8</a> |
| Principle document of DC-to-DC converter manual | Build club website DC to DC project                                     |

## Aim

Very often a low power boost converter used to convert some low voltage to a higher voltage is required in a system. This build exercise is to learn to build one such simple converter, using an open loop.

## Components

| Components     | Specification                         | Cost Per Quantity | Quantity |
|----------------|---------------------------------------|-------------------|----------|
| PCB Dot board  | 10*15cm                               | 40                | 1        |
| Inductor       | 1mH                                   | 50                | 1        |
| Capacitor      | 100-470uf (63V)                       | 25                | 1        |
| MOSFET         | IRLZ24NPBF<br>OR<br>NVMFS6H818NL      | 160               | 1        |
| Schottky Diode | STPSC406D<br>OR<br>NXPSC046506Q<br>OR | 150               | 1        |




|                                    |                               |     |            |
|------------------------------------|-------------------------------|-----|------------|
|                                    | WNSC6D04650Q                  |     |            |
| DC Fan (Load)                      | 12V- 0.27A                    | 95  | 1          |
| Resistor                           | 1K,2K,340K ohm (Through hole) | 15  | 3 Each one |
| Soldering station (Lead, flux, IP) |                               | 250 | 1          |
| Power supply                       | 5V Phone Adapter              | 100 | 1          |
| Connecting wires                   | 26AWG                         | 20  | 1(meter)   |
| Bread board                        | 400 pins                      | 50  | 1          |
| Digital multimeter                 |                               | 175 | 1          |
| Jumper wire Male to male           |                               | 15  | 6          |
| Dexter board                       |                               |     | 1          |
| USB cable                          | Type B                        | 200 | 2          |

Note:

- All the components are reusable after desoldering.
- Measure the resistor values by multimeter.



Inductor

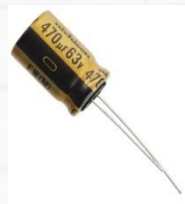

Capacitor



MOSFET



Schottky Diode



Jumper wires




USB cable



Power supply



Resistor

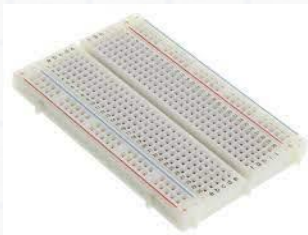

Bread Board



DOT Board



Soldering station




Dexter Board

**MOSFET PINOUT:**

Pin 1 = gate


Pin 2 = drain

Pin 3 = source

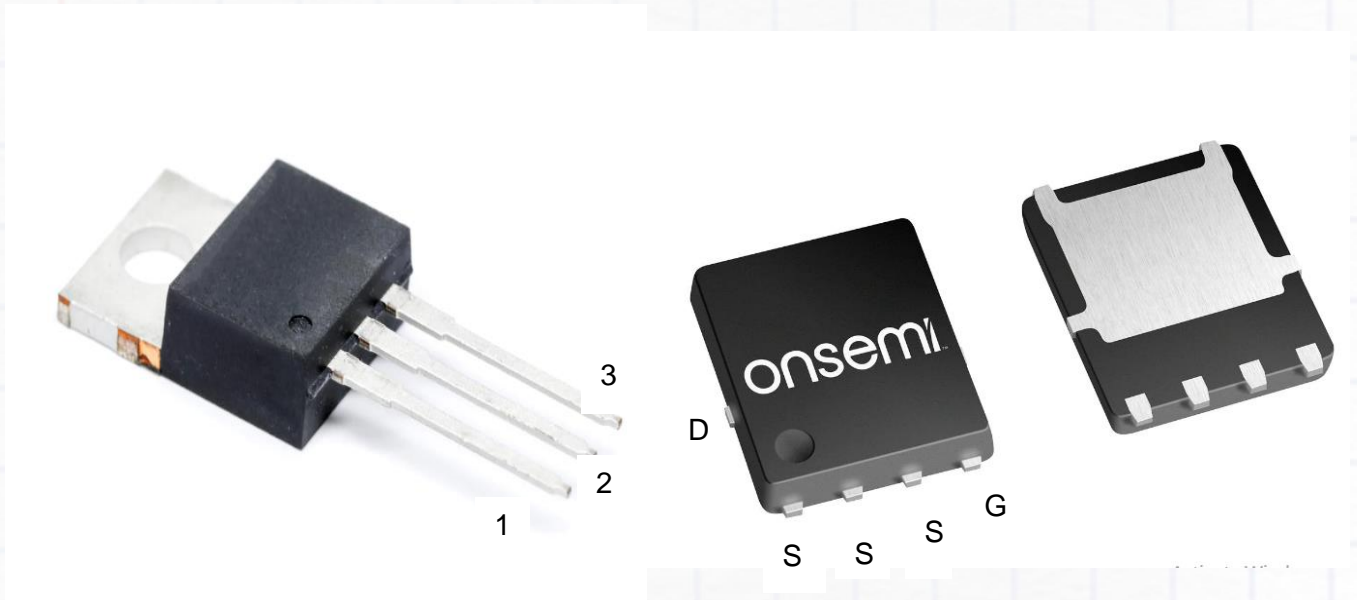

**IRLZ24NPBF**

**NVMFS6H818NL**

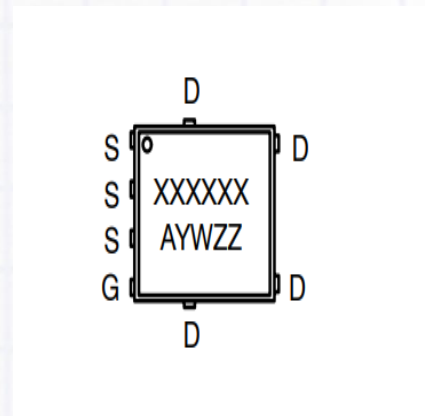


Note: While choosing the MOSFET, check from the datasheet that MOSFET  $V_{gs}$  should be less than 2.5V.

## Connections
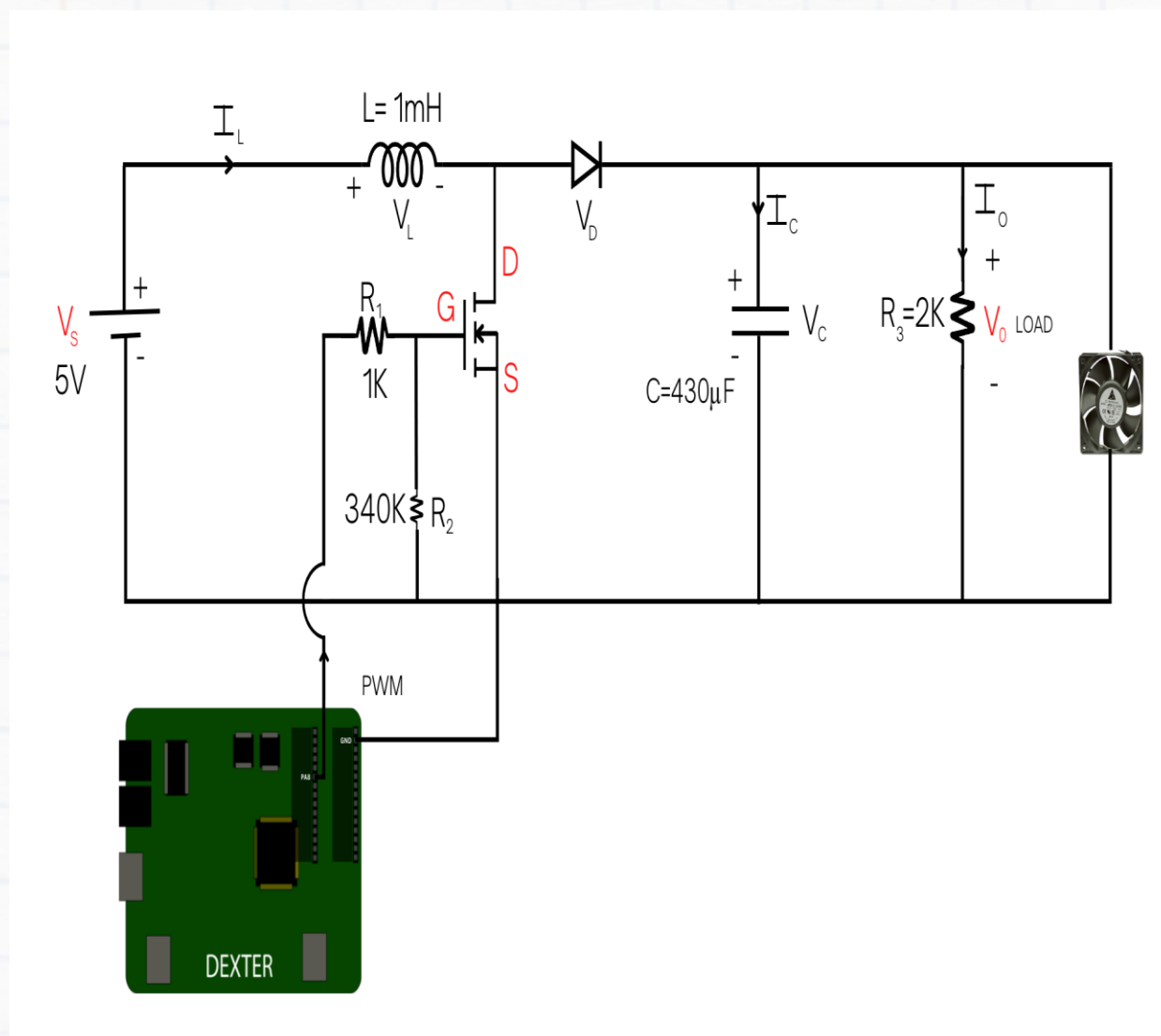
### Circuit Diagram

**NOTE:** First make the circuit diagram in the Bread board and verify the connection properly once you got the output then only go for soldering. Do not touch the tip of the soldering iron, its temperature can be as high as  $380^{\circ}\text{C}$  and can cause severe burns. Keep the cleaning sponge wet when soldering.








- Connect or Solder one male to male jumper wire to the MOSFET **gate** and connect another side of jumper wire to **PA8 pin** of Dexter.
- Connect or Solder one male to male jumper wire to the **MOSFET source** and connect another side of jumper wire to **GND pin** of Dexter.

**Step 5:** Connect 1K resistor between gate of the MOSFET and PA8 of the Dexter board.

**Step 6:** Connect 340K resistor between gate of the MOSFET and GND of the Bread board.

**Step 7:** Connect 2K resistor parallel to the capacitor.

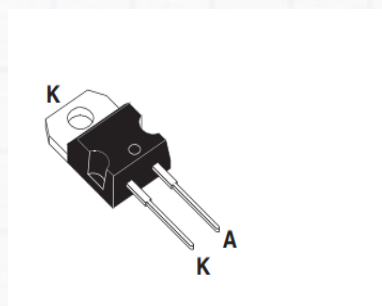**Step 8:** Connect or Solder anode of the diode to point **B**. And cathode **C** of the diode to positive of the capacitor.



K = cathode

A = anode

- **Negative side** of capacitor to the ground (G).
- Connect (**C**) with one leg of resistor and another with (G).

**Step 9:** Connect or solder two male to male jumper wire across the capacitor and connect to the 12V DC load fan.




**Step 10:** Switch ON the power supply and measure the output voltage using digital multimeter across the capacitor.

**Step 11:** To change the duty cycle write two commands in STM IDE.

## Software

### Downloads & Installation

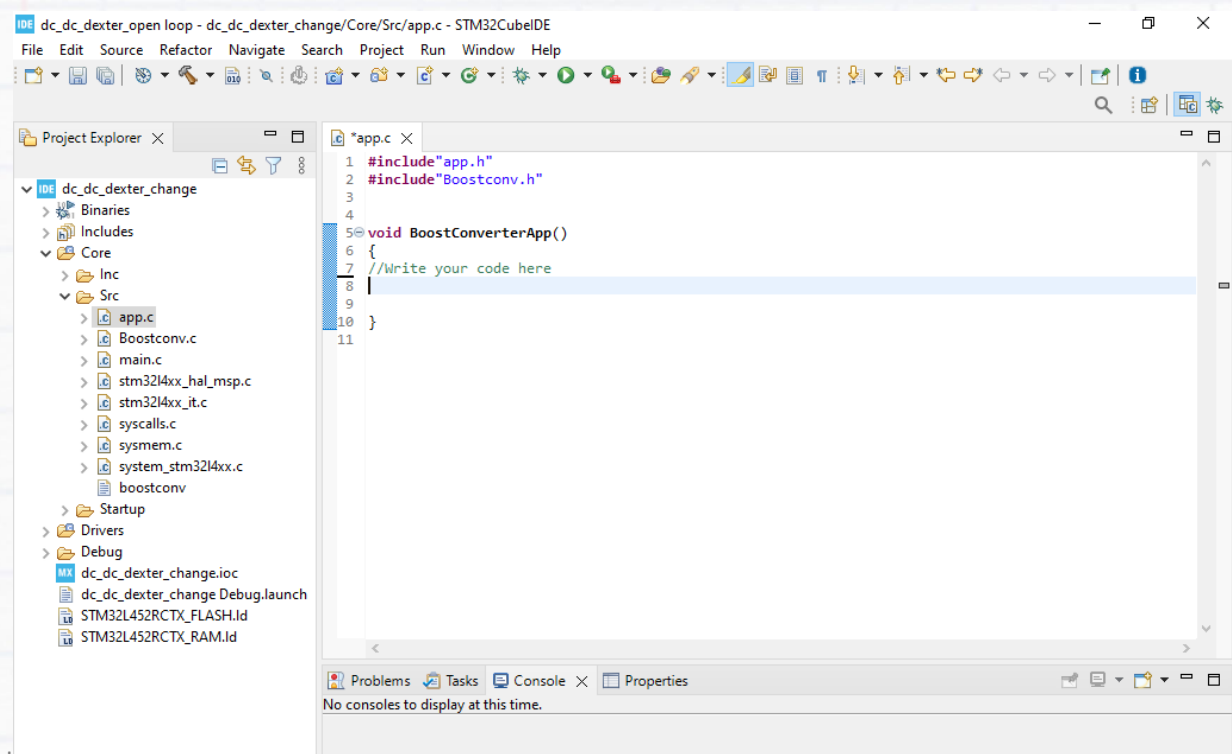- 1) Download the Project Workspace file '**dc\_dc\_dexter\_open loop.zip**' given in the project page on the Build Club website.
- 2) Then go in downloads and extract all.
- 3) i) Launch the STM IDE, ii) click on Import project iii) Now click on the directory and select the extracted file **dc\_dc\_dexter\_open loop** iv) Click on **dc\_dc\_dexter\_change** then **core** then **src** and then **app.c**



## Implementing the Code

Write the following command to change the period and duty cycle and run the code.

```

1 #include"app.h"
2 #include"Boostconv.h"
3
4
5 void BoostConverterApp()
6 {
7 //Write your code here
8     Set_Period(200);
9     Set_Duty(116 ); // for 58% duty cycle
10
11
12 }
13

```

- The **Set\_Period( )** function allows you to change the frequency.  
To change Period =  $\frac{\text{system clock frequency}}{\text{required frequency}}$

**Note:** system clock frequency will always be 4MHz

Example: Change frequency to 20KHz

$$\text{Period} = \frac{4\text{MHz}}{20\text{KHz}} = 200$$

**Set\_Period(200);** // for 20KHz frequency



- The **Set\_Duty( )** function allows you to change the duty cycle.

To change Duty = period  $\times$  (%percentage of duty cycle)

Example: Change duty cycle to 58%

$$\begin{aligned} \text{Duty} &= 200 \times (58/100) \\ &= 116 \end{aligned}$$

**Set\_Duty(116);** // for 58% duty cycle

Hurray you have learnt how to drive a boost circuit!!!!!!

### Tasks: for open loop

1. On the same boost converter change the duty cycle 50%, 60% and 70% keeps the frequency 20Khz and measure the voltage.
2. Measure the output voltage keeping  $R = 12\text{ohm}$ . Compute the expected voltage using mathematical formula for each of the duty cycle. Check measure voltage and compute voltage are matching.

### Exercise:

1. Calculate the losses and the efficiency using the formula.
2. Make a graph
  - between ripple voltage and duty
  - between ripple voltage and load